

Part 3

lesson

2

**74HC595 And
Segment Display**

Overview

In this lesson ,we will use the 74HC595 shift register to control the segment display.

The segment display will show number from 0-9.

Component Required:

- (1) x Elegoo Uno R3
- (1) x 830 tie-points breadboard
- (1) x 74HC595 IC
- (1) x 1 Digit 7-Segment Display
- (8) x 220 Ω resistors
- (26) x M-M wires (Male to Male jumper wires)



Component Introduction


Seven segment display

Below is the segment pin diagram.


0-9 ten digits correspond with each segment are as follows (the following table applies common cathode seven segment display device, if you are using a common anode, the table should be replaced every 1 0 (1->0,0->1).

0 should all replaced by 1


1 should all replaced by 0:

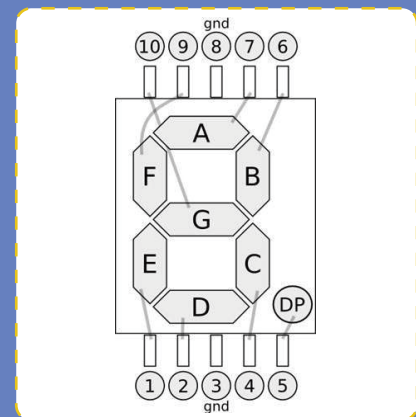

Display digital	dp	a	b	c	d	e	f	g
0	0	1	1	1	1	1	1	0
1	0	0	1	1	0	0	0	1
2	0	1	1	0	1	1	0	1
3	0	1	1	1	1	0	0	1
4	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1
6	0	1	0	1	1	1	1	1
7	0	1	1	1	0	0	0	0
8	0	1	1	1	1	1	1	1
9	0	1	1	1	1	0	1	1

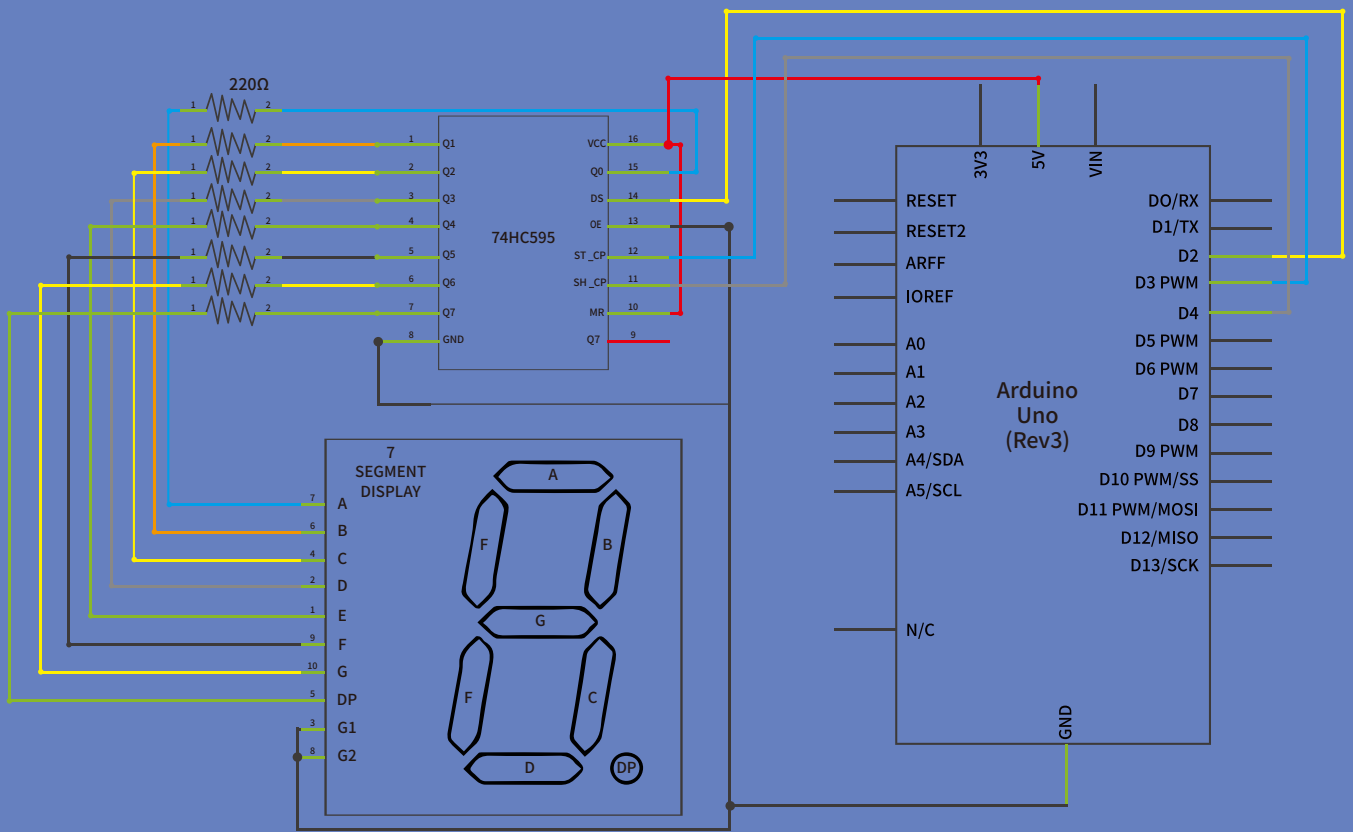

Connection Schematic

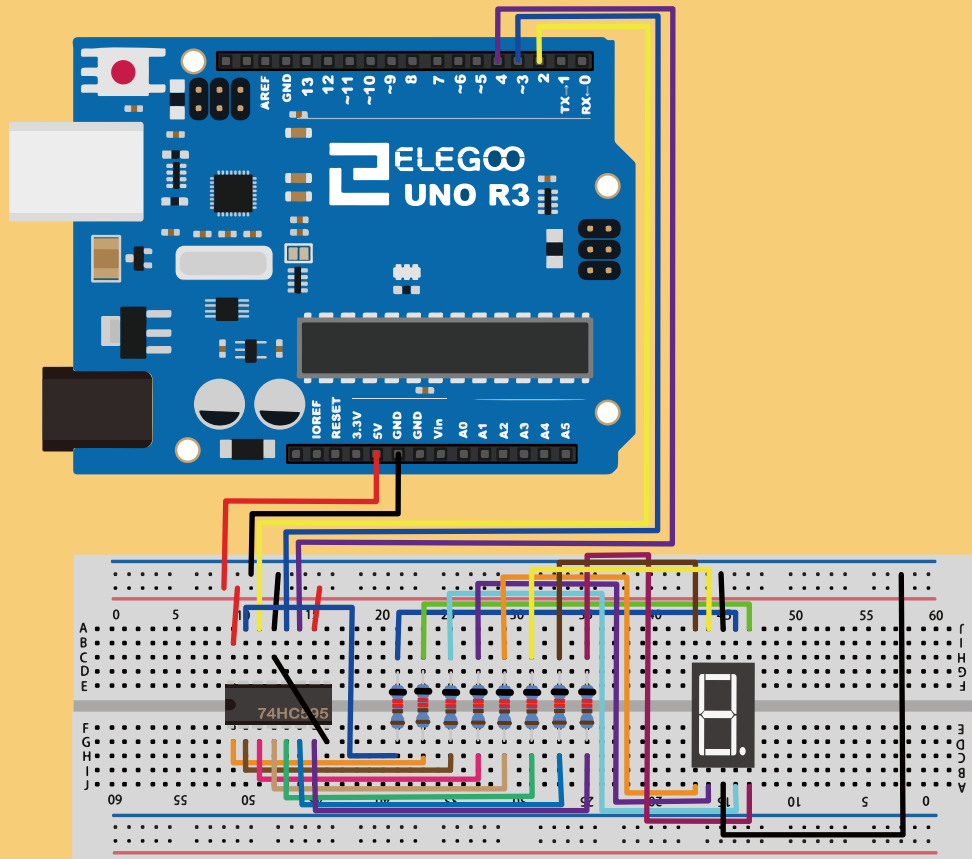

Wiring diagram

The following table shows the seven-segment display 74HC595 pin correspondence table:

Step one: Connect 74HC595

First, the wiring is connected to power and ground:

VCC (pin 16) and MR (pin 10) connected to 5V

GND (pin 8) and OE (pin 13) to ground

Connection DS, ST_CP and SH_CP pin:

DS (pin 14) connected to UNO R3 board pin 2 (the figure below the yellow line)

ST_CP (pin 12, latch pin) connected to UNO R3 board pin 3 (FIG blue line below)

SH_CP (pin 11, clock pin) connected to UNO R3 board pin 4 (the figure below the white line)

Step two: Connect the segment display

The seven-segment display 3 and 8 pins to the UNO R3 boards GND. (This example uses the common cathode, if you use the common anode, please connect 3 and 8 pins pin to UNO R3 board + 5V)

According to the table above, connect the 74HC595 Q0 ~ Q7 to seven-segment display corresponding pin (A ~ G and DP), and then each lead in a 220Ω resistor in series..

74HC595 pin	Seven shows remarkable control pin (stroke)
Q0	7 (A)
Q1	6(B)
Q2	4(C)
Q3	2 (D)
Q4	1 (E)
Q5	9 (F)
Q6	10(G)
Q7	5(DP)

Code

After wiring, please open the program in the code folder- **74HC595_And_Segment_Display** And Segment Display and click UPLOAD to upload the program. See Lesson 5 of part 1 for details about program uploading if there are any errors.